

1.) Determine $\mathbf{H}(\omega) = \mathbf{V}_o(\omega)/\mathbf{V}_i(\omega)$ and sketch the asymptotic Bode magnitude plot for the circuit shown in Figure 1.

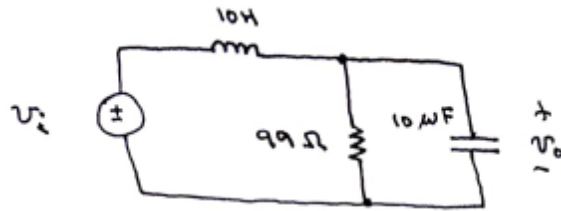


Figure 1

2.) Determine $\mathbf{H}(\omega) = \mathbf{V}_o(\omega)/\mathbf{V}_i(\omega)$ and sketch the asymptotic Bode magnitude plot for the circuit shown in Figure 2.

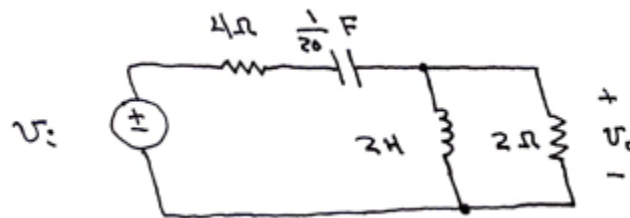


Figure 2

3.) Determine $\mathbf{H}(\omega) = \mathbf{V}_o(\omega)/\mathbf{V}_i(\omega)$ and sketch the asymptotic Bode magnitude plot for the circuit shown in Figure 3.

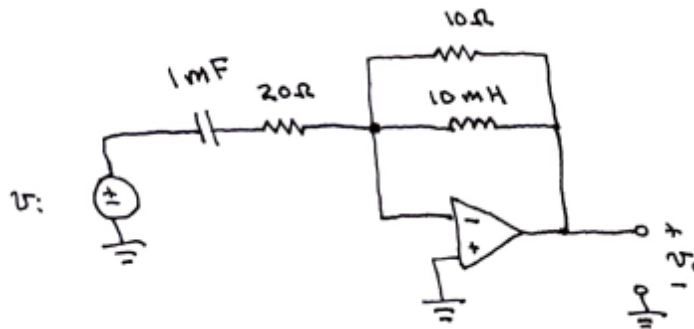


Figure 3

4.) (a) Sketch the asymptotic Bode magnitude plot for a circuit with network function

$$\mathbf{H}(\omega) = \frac{12000000j\omega}{(j\omega+300)(j\omega+4000)}$$

(b) Plot the exact Bode magnitude plot using Matlab

5.) (a) Sketch the asymptotic Bode magnitude plot for a circuit with network function

$$\mathbf{H}(\omega) = \frac{1600000(j\omega+400)(j\omega+8000)}{(j\omega+20)(j\omega^2+j\omega+100000)}$$

(b) Plot the exact Bode magnitude plot using Matlab

6.) Determine the maximum value of $|\mathbf{H}(\omega)|$, the resonant frequency, the bandwidth, and the quality factor for the parallel resonant circuit shown in Figure 4. Sketch the asymptotic Bode magnitude plot.

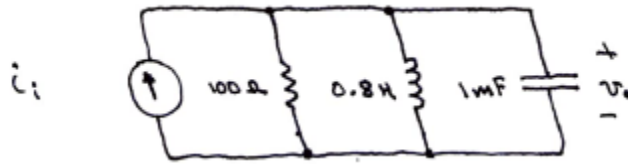


Figure 4

7.) Design the series resonant circuit shown in Figure 5 to have the network function $\mathbf{H}(\omega) = \frac{j\omega/3}{(j\omega)^2 + 2j\omega + 101}$. Sketch the asymptotic Bode magnitude plot. Determine the resonant frequency, the bandwidth, and the quality factor for the circuit.

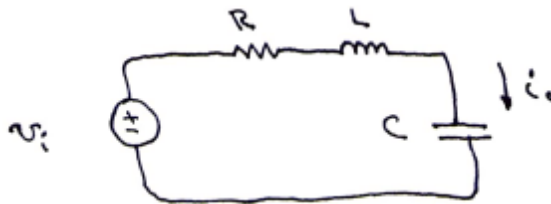


Figure 5