# ECE426/516 Lab 2

Professor: Chao Lu Email: chaolu@siu.edu

# ECE 426/516 Implementation of VLSI Systems with HDL Lab 2 3-8 Decoder

## **Lab Description**

In this lab section, you will design a BCD to decimal decoder (3-8 decoder) in both structural and behavioral Verilog codes, synthesis your designs and run simulations.

## **Lab Introduction**

Table 1 is the truth table for BCD to decimal decoder

| Table 1 Gray Code for each Binary Code word |            |       |       |         |       |       |       |       |       |       |       |
|---|------------|-------|-------|---------|-------|-------|-------|-------|-------|-------|-------|
| Enable                                      | BCD Inputs |       |       | Outputs |       |       |       |       |       |       |       |
| en  | $i_2$      | $i_1$ | $i_0$ | $d_0$   | $d_1$ | $d_2$ | $d_3$ | $d_4$ | $d_5$ | $d_6$ | $d_7$ |
| 1   | 0          | 0     | 0     | 1       | 0     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1   | 0          | 0     | 1     | 0       | 1     | 0     | 0     | 0     | 0     | 0     | 0     |
| 1   | 0          | 1     | 0     | 0       | 0     | 1     | 0     | 0     | 0     | 0     | 0     |
| 1   | 0          | 1     | 1     | 0       | 0     | 0     | 1     | 0     | 0     | 0     | 0     |
| 1   | 1          | 0     | 0     | 0       | 0     | 0     | 0     | 1     | 0     | 0     | 0     |
| 1   | 1          | 0     | 1     | 0       | 0     | 0     | 0     | 0     | 1     | 0     | 0     |
| 1   | 1          | 1     | 0     | 0       | 0     | 0     | 0     | 0     | 0     | 1     | 0     |
| 1   | 1          | 1     | 1     | 0       | 0     | 0     | 0     | 0     | 0     | 0     | 1     |
| 0   | X          | X     | X     | 0       | 0     | 0     | 0     | 0     | 0     | 0     | 0     |

Table 1 Gray Code for each Binary Code Word

Figure 1 is the block diagram of a 3:8 decoder with an enable pin.

 


Figure 1 Block diagram of a 3:8 decoder

#### Lab Procedure

Please read and follow the underneath instructions to finish your lab.

1. Structural design of a 3:8 decoder with an enable signal (en), by instantiating AND, OR, and INV gates which are Verilog primitive gates. You should not use an always statement in your structural design. Use the following module template for your decoder design.

```
module decoder_3_8_structural (en, i, d);
input en;
input [2:0] i;
output [7:0] d;
wire [2:0] i_;

// start your code here
endmodule
```

- 2. Test your structural design by exhaustively run simulation of all possible input combinations (16 combinations in total).
- 3. Behaviorally design the same 3:8 decoder using a single always procedure. Hint: you can use an if-then-else statement to implement the enable functionality. Use the following module template for your decoder design.

```
module decoder_3_8_behavioral(en, i, d);
input [2:0] i;
input en;
output [7:0] d;
reg [7:0] d;

// start your code here
endmodule
```

4. Test your behavioral design by exhaustively simulating all possible input combinations (16 combinations in total). Ensure that your behavioral design behaves the same as your structural design.

We strongly recommend coding by yourself, although the code below is a reference.

#### Lab Guide

1. Create a new directory named 'lab2', using 'mkdir' command like this: /home/grad/siu854024310/ECE426-45> mkdir lab2

Change your working directory to "lab2". You can download 5 reference codes from D2L and upload them into this lab2 folder.

```
/home/staff/eeluchao/ECE426/lab2-53> ls
decoder_3_8_behavioral.v run_dc_behavioral.tcl testbench.v
decoder_3_8_structural.v run_dc_structural.tcl
/home/staff/eeluchao/ECE426/lab2-54> ■
```

2. The structural code (decoder\_3\_8\_structural.v) uses only primitive gates, and the behavioral code (decoder\_3\_8\_behavioral.v) uses case-statements.

```
module decoder 3 8 structural (en, i, d);
input en;
input [2:0] i;
output [7:0] d;
wire [2:0] i ;
not N0 (i [0], i[0]);
not N1 (i [1], i[1]);
not N2 (i_[2], i[2]);
and A0 (d[0], en, i_[2], i_[1], i_[0]);
and A1 (d[1], en, i_[2], i_[1], i[0]);
and A2 (d[2], en, i[2], i[1], i[0]);
and A3 (d[3], en, i [2], i[1], i[0]);
and A4 (d[4], en, i[2], i[1], i[0]);
and A5 (d[5], en, i[2], i[1], i[0]);
and A6 (d[6], en, i[2], i[1], i [0]);
and A7 (d[7], en, i[2], i[1], i[0]);
endmodule
```

```
module decoder_3_8_behavioral(en, i, d);

input [2:0] i;
input en;
output [7:0] d;
reg [7:0] d;
always @ (en or i)

begin
case({en, i})
4'b0XXX: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end
4'b1000: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 1; end
4'b1001: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 1; d[0] = 0; end
4'b1010: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 1; d[1] = 0; d[0] = 0; end
4'b1011: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 1; d[2] = 0; d[1] = 0; d[0] = 0; end
```

```
4'b1100: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 1; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end 4'b1101: begin d[7] = 0; d[6] = 0; d[5] = 1; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end 4'b1110: begin d[7] = 0; d[6] = 1; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end 4'b1111: begin d[7] = 1; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end default: begin d[7] = 0; d[6] = 0; d[5] = 0; d[4] = 0; d[3] = 0; d[2] = 0; d[1] = 0; d[0] = 0; end endcase end endmodule
```

#### 3. Write testbench.v to run simulation.

```
`include "decoder 3 8 structural.v"
'include "decoder 3 8 behavioral.v"
module testbench();
reg [2:0] inputs;
reg enable;
wire [7:0] o structural;
wire [7:0] o behavioral;
initial
begin: apply stimulus
reg [4:0] invect;
for (invect = 0; invect <= 16; invect = invect + 1)</pre>
        {enable, inputs[2], inputs[1], inputs[0]} = invect[4:0];
        #10 $monitor ("#structural# enable = %b, inputs inputs[2:0]=%b, outputs
d[7:0]=%b", enable, inputs[2:0], o structural[7:0]);
        #10 $monitor ("#behavioral# enable = %b, inputs inputs[2:0]=%b, outputs
d[7:0]=%b", enable, inputs[2:0], o_behavioral[7:0]);
   end
end
decoder 3 8 structural inst s (
.en(enable),
.i(inputs),
.d(o structural)
decoder 3 8 behavioral inst b (
.en(enable),
.i(inputs),
.d(o behavioral)
);
endmodule
```

4. Type command 'synopsys' to enter Synopsys shell. This may take a few minutes.

To check if you are in the synopsys shell environment, you can check using command 'which dc\_shell', if the return of such command popped up is like below, then you have successfully entered synopsys shell.

```
/home/staff/eeluchao/ECE426/lab2-55> synopsys
/home/staff/eeluchao/ECE426/lab2-56> which dc_shell
/synopsys/Design_Compiler/syn/S-2021.06-SP5-4/bin/dc_shell
/home/staff/eeluchao/ECE426/lab2-57> ■
```

Vlogan the design: type "vlogan decoder 3 8\_behavioral.v"

Vlogan the design: type "vlogan decoder\_3\_8\_structural.v"

```
/home/staff/eeluchao/ECE426/lab2-59> vlogan decoder_3_8_structural.v
                                 Chronologic VCS (TM)
             Version T-2022.06-SP1 -- Wed Jan 25 18:57:37 2023
                          Copyright (c) 1991 - 2022 Synopsys, Inc.
    This software and the associated documentation are proprietary to Synopsys,
 Inc. This software may only be used in accordance with the terms and conditions
 of a written license agreement with Synopsys, Inc. All other use, reproduction, or distribution of this software is strictly prohibited. Licensed Products communicate with Synopsys servers for the purpose of providing software updates, detecting software piracy and verifying that customers are using Licensed Products in conformity with the applicable License Key for such
  Licensed Products. Synopsys will use information gathered in connection with
     this process to deliver software updates and pursue software pirates and
                                               infringers.
 Inclusivity & Diversity - Visit SolvNetPlus to read the "Synopsys Statement on
                Inclusivity and Diversity" (Refer to article 000036315 at
                                https://solvnetplus.synopsys.com)
Parsing design file 'decoder_3_8_structural.v'
CPU time: .142 seconds to compile
/home/staff/eeluchao/ECE426/lab2-60>
```

Vlogan the testbench: type "vlogan testbench.v"

Type 'vcs testbench.v -debug\_acc+all -debug\_region+cell+encrypt -kdb"

Run './simv -gui' to see the testbench output in a graphic environment tool verdi.

```
/home/staff/eeluchao/ECE426/lab2-77> ./simv -gui
logDir = /home/staff/eeluchao/ECE426/lab2/verdiLog

Verdi (R)


Version T-2022.06-SP2-1 for linux - Jan 12, 2023

Copyright (c) 1999 - 2023 Synopsys, Inc.


This software and the associated documentation are proprietary to Synopsys,
Inc. This software may only be used in accordance with the terms and conditions
of a written license agreement with Synopsys, Inc. All other use, reproduction,
or distribution of this software is strictly prohibited. Licensed Products
communicate with Synopsys servers for the purpose of providing software
updates, detecting software piracy and verifying that customers are using
Licensed Products in conformity with the applicable License Key for such
Licensed Products. Synopsys will use information gathered in connection with
this process to deliver software updates and pursue software pirates and
infringers.

Inclusivity & Diversity - Visit SolvNetPlus to read the "Synopsys Statement on
Inclusivity and Diversity" (Refer to article 000036315 at
https://solvnetplus.synopsys.com)
rcfile = /synopsys/VERDI_2022/verdi/T-2022.06-SP2-1/etc/novas.rc
guiConfFile (read) = /home/staff/eeluchao/ECE426/lab2/novas.conf (working directory)
guiConfFile (write) = /home/staff/eeluchao/ECE426/lab2/novas.conf (working directory)
**WARN* Verdi-Elite (Verdi) license is not available. Try to check out Verdi-Apex (Verdi-Ultra) license.
```

 5. See the waveforms of your design. To generate a waveform, click on "Tools > New Waveform".



 6) Drag the instance that is being simulated (e.g. inst\_b, inst\_s) and drop it on the left black window/panel. Finally, to run the simulation, go to "Simulation >Run/Continue". The results (waveforms) can be observed in the larger (right) window/panel.



### Demo

You should demo the following aspects of your design, and include the following 5 items in your report.

- 1. Verilog code for structural 3:8 decoder design.
- 2. Simulation waveforms demonstrating correct functionality of the structural 3:8 decoder design
- 3. Verilog code for behavioral 3:8 decoder design.
- 4. Simulation waveforms demonstrating correct functionality of the behavioral 3:8 decoder design
- 5. Synthesize one of your design and capture the reported performance (area and power).