

**Question 1:** for the combinational circuit shown in Figure 1,

- Write the Boolean expression of  $T_1$ ,  $T_3$ ,  $T_4$ ,  $F_1$  and  $F_2$  in terms of the four input variables  $A$ ,  $B$ ,  $C$ ,  $D$ .
- Write the truth table showing binary values of  $T_1$ ,  $T_3$ ,  $T_4$ ,  $F_1$  and  $F_2$  for all combinations of four inputs ( $A$ ,  $B$ ,  $C$ ,  $D$ )
- Simplify the functions of  $F_1$  and  $F_2$  by using Karnaugh map method.

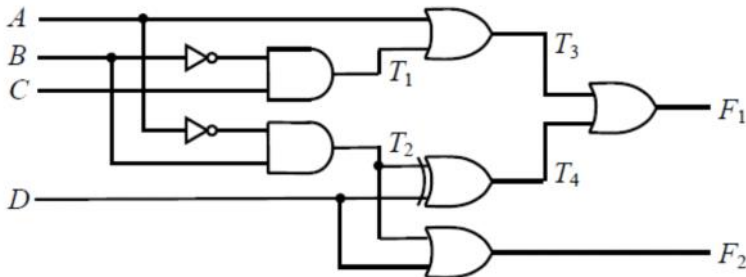


Figure 1. Combinational circuit

BOOLEAN EXPRESSIONS

$$T_1 = \overline{B}C$$

$$T_3 = A + \overline{B}C$$

$$T_4 = D \oplus \overline{A}C$$

$$F_1 = (A + \overline{B}C) + (D \oplus \overline{A}C)$$


$$F_2 = \overline{A}C + D$$

② TRUTH TABLE

ABCD	T1	T3	T4	F1	F2
0000	0	0	0	0	0
0001	0	0	1	1	1
0010	1	1	0	1	0
0011	1	1	0	1	1
0100	0	0	1	1	1
0101	0	0	0	0	1
0110	0	0	1	1	1
0111	0	0	0	0	1
1000	0	1	0	1	0
1001	0	1	1	1	1
1010	1	1	0	1	0
1011	1	1	1	1	1
1100	0	1	0	1	0
1101	0	1	1	1	1
1111	0	1	1	1	1

③ KMAPS FOR  $F_1$  and  $F_2$


$F_1$

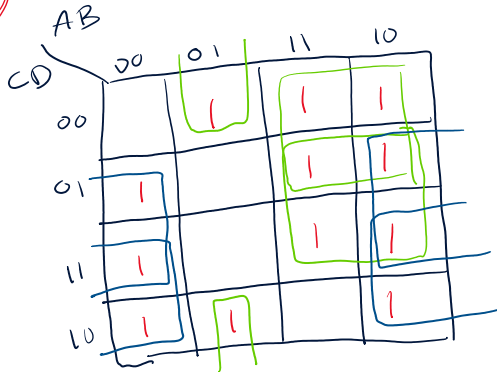

⑤ groups

$$F_1 = \overline{B}D + \overline{B}C + \overline{A}B\overline{D} + A\overline{C} + AD$$

$F_2$

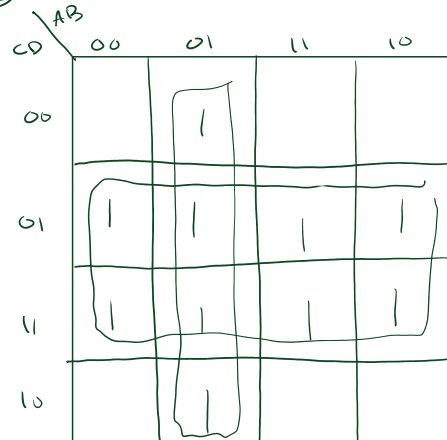

② groups

$$F_2 = D + \overline{A}B$$

**Question 2:** consider the following sequential building blocks in Figure 2,

- What type of sequential block is it?
- Assume that  $S = R = 1$ , what happens to the outputs  $Q$  and  $Q'$  when  $CLK$  transitions from a 1 to 0?


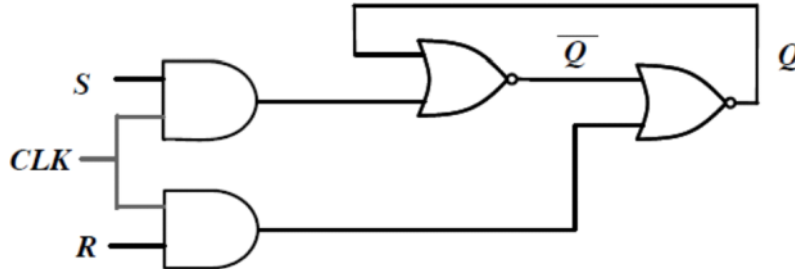


Figure 2 Sequential circuit


(A)

Redrawing the circuit

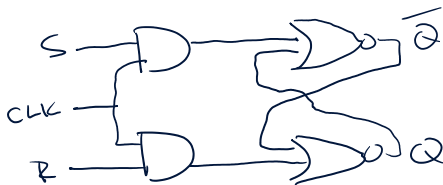

We can see this is  
an SR Latch

(B)

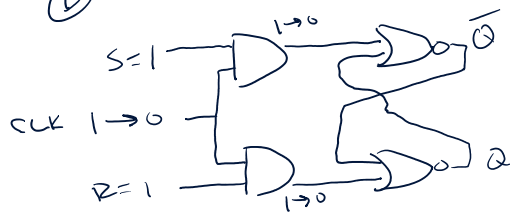

$$\overline{Q} = \overline{Q + 0} = \overline{Q}$$

$$Q = \overline{\overline{Q} + 0} = \overline{\overline{Q}} = Q$$

In this state the outputs  
are held as their previous  
values

**Question 3:** the circuit in Figure 3 looks like a counter. What is the sequence that this circuit counts in? Complete the timing diagram given in Figure 3. The initial conditions of  $Q_0Q_1Q_2$  are 000.



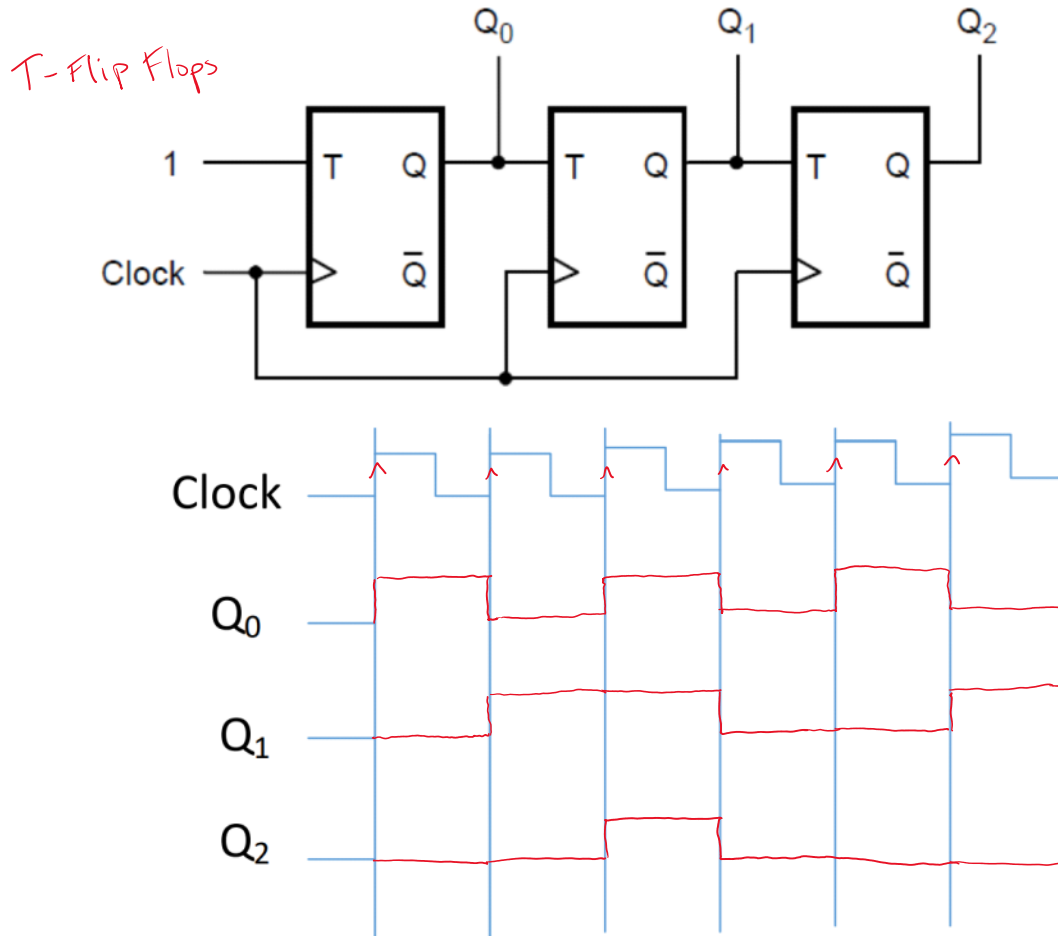


Figure 3. Counter-type circuit

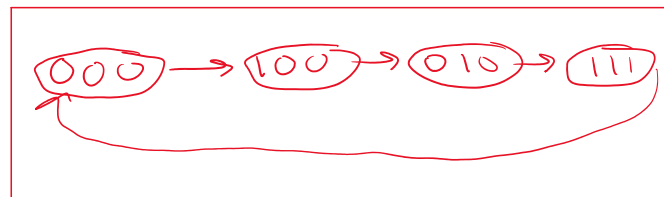*The sequence we see out of this counter, where its in the form  $Q_0Q_1Q_2$  is,*



**Question 4:** you are given the sequential circuit shown in Figure 4. Find the state diagram, state assigned table and state table for the circuit using Mealy-type FSM. Assume the state assignments as  $\{A=00, B=01, C=10, D=11\}$ .

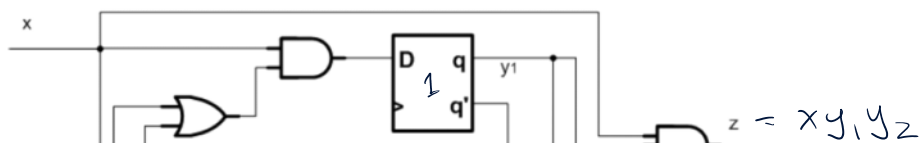

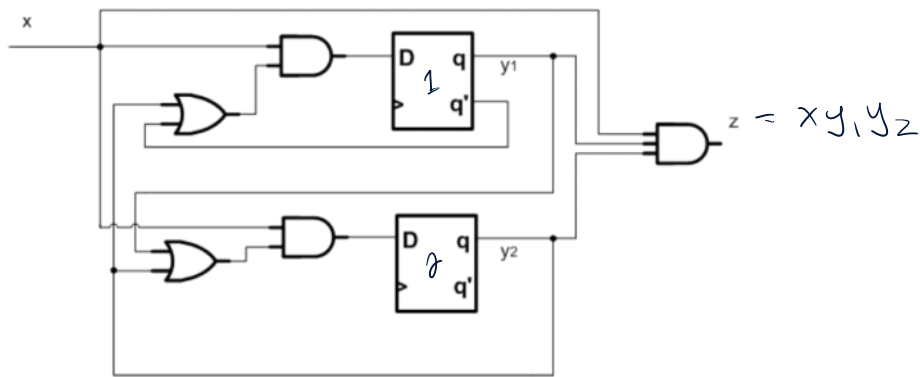


Figure 4. Finite-State Machine circuit

$$D_1 = x(\bar{y}_1 + y_2)$$

B/c D FF,  
we know

$$D_2 = x(y_1 + y_2)$$

$$Q_{t+1} = D$$

$$y_{1,t+1} = x(\bar{y}_1 + y_2) = x\bar{y}_1 + xy_2$$

$$y_{2,t+1} = x(y_1 + y_2) = xy_1 + xy_2$$

$$z = xy_1y_2$$

STATE TRANSITION TABLE

PRESENT STATE		INPUT $x$	NEXT STATE		OUTPUT $z$
$y_1$	$y_2$		$y_{1,t+1}$	$y_{2,t+1}$	
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	0	0
0	1	1	1	1	0
1	0	0	0	0	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	1	1	1

$\Rightarrow$

P.S. $y_1y_2$	INPUT $x$	N.S. $y_1^+y_2^+$	OUTPUT $z$
A	0	A	0
A	1	C	0
B	0	A	0
B	1	D	0
C	0	A	0
C	1	B	0
D	0	A	0
D	1	D	1

STATE DIAGRAM

\*unless specified,  $z=0$ .

