

ROM Squarer and Square Rooter Circuits

Verilog Lab 5

Chase A. Lotito, *SIUC Undergraduate*

Section A: Squaring Circuit

The following Verilog code implements a read-only memory (ROM) block that stores data for the squares of numbers; specifically, the squares for unsigned numbers 0 to 15, and signed numbers -8 to +7.

```
1  /*
2     Chase Lotito - SIUC
3     ECE426 - Lab 5 - Design of Memory in Verilog
4     Section A: ROM Squaring Circuit
5         -> square unsigned 0-15
6         -> square signed -8-7
7  */
8
9  module rom_a (n, sign, square);
10
11     // I/O
12     input [3:0] n;           // signed number
13     input sign;             // bit (1 = signed) (0 = unsigned)
14     output reg [7:0] square; // answer = n**2
15
16     // procedural block to compute squares as inputs come in
17     always @ (n or sign)
18     begin
19         if (sign == 1'b0)
20         begin
21             case (n)          // UNSIGNED
22                 0 : square <= 0;
23                 1 : square <= 1;
24                 2 : square <= 4;
25                 3 : square <= 9;
26                 4 : square <= 16;
27                 5 : square <= 25;
28                 6 : square <= 36;
29                 7 : square <= 49;
30                 8 : square <= 64;
31                 9 : square <= 81;
32                 10 : square <= 100;
33                 11 : square <= 121;
34                 12 : square <= 144;
35                 13 : square <= 169;
36                 14 : square <= 196;
37                 15 : square <= 225;
```

```

38         default: square <= 1'bx; // invalid input
39     endcase
40 end
41 else
42 begin
43     case(n) // SIGNED
44         0 :square <= 0;
45         1 :square <= 1;
46         2 :square <= 4;
47         3 :square <= 9;
48         4 :square <= 16;
49         5 :square <= 25;
50         6 :square <= 36;
51         7 :square <= 49;
52         8 :square <= 64; // -8 x -8
53         9 :square <= 49;
54         10 :square <= 36;
55         11 :square <= 25;
56         12 :square <= 16;
57         13 :square <= 9;
58         14 :square <= 4;
59         15 :square <= 1;
60         default: square <= 1'bx; // invalid input
61     endcase
62 end
63 end
64
65 endmodule

```

To simulate the functionality of this ROM block, I sent in binary values 0000 to 1111 twice, where one iteration has the sign-bit set to 0 (unsigned) and then the sign-bit set to 1 (signed).

```

1  /*
2      chase lotito
3      lab 5 section a
4      rom squarer testbench
5  */
6
7  `include "./rom_a.v"
8  `timescale 1us / 1us
9
10 module rom_a_tb();
11
12 // GTKWAVE (waveform simulator)
13 initial begin : GTKWAVE
14     $dumpfile("rom_a.vcd");
15     $dumpvars(0, rom_a_tb);

```

```

16 end
17
18 // I/O
19 reg [3:0] n;           // signed number
20 reg sign;             // bit (1 = signed) (0 = unsigned)
21 wire [7:0] square;    // answer = n**2
22
23 // Initialize the Squarer ROM
24 rom_a U1 (
25     .n(n), .sign(sign), .square(square)
26 );
27
28 // Send 4-bit numbers 0000 -> 1111
29 initial begin : stimulus
30
31     // begin sim with unsigned numbers
32     sign = 0;
33
34     // n = 0000 -> 1111
35     for(integer i = 0; i < 16; i = i + 1)
36         #10 n = i;
37
38     #10 n = 0;        // reset n
39     sign = 1;         // flip to signed
40     #20;              // small delay til next loop
41
42     // n = 0000 -> 1111
43     for(integer i = 0; i < 16; i = i + 1)
44         #10 n = i;
45
46     #10 $finish;
47 end
48
49
50 endmodule

```

This gave the following waveforms in GTKWAVE:

 


Figure 1: Squarer Circuit Output Waveforms

Section B: Square Rooting Circuit

The following Verilog code implements a read-only memory (ROM) block that stores data for the square roots of 0 to 15 (unsigned). Since we cannot set a register directly to a decimal with a non-integer value, we will set the register to a concatenated version containing the integer part and the decimal part, then use a continuous assignment to extract that information after the ROM has been accessed.

```

1  /*
2     Chase Lotito - SIUC
3     ECE426 - Lab 5 - Design of Memory in Verilog
4     Section B: ROM Square Root Circuit
5     -> sq_root root unsigned 0-15
6     -> provide 3 decimals
7  */
8
9  module rom_b (n, sq_root);
10
11  // I/O
12  input [3:0] n;           // unsigned number
13  output reg [11:0] sq_root; // answer = n**1/2
14
15  wire [1:0] sq_root_int;   // integer part of sq_root
16  wire [9:0] sq_root_dp;   // decimal part of sq_root
17
18  // procedural block to compute roots as inputs come in
19  always @ (n)
20  begin
21      case (n)
22          0 :sq_root <= 0;
23          1 :sq_root <= {2'd1, 10'd0};
24          2 :sq_root <= {2'd1, 10'd414};
25          3 :sq_root <= {2'd1, 10'd732};
26          4 :sq_root <= {2'd2, 10'd0};
27          5 :sq_root <= {2'd2, 10'd236};
28          6 :sq_root <= {2'd2, 10'd450};
29          7 :sq_root <= {2'd2, 10'd646};
30          8 :sq_root <= {2'd2, 10'd828};
31          9 :sq_root <= {2'd3, 10'd0};
32          10 :sq_root <= {2'd3, 10'd162};
33          11 :sq_root <= {2'd3, 10'd317};
34          12 :sq_root <= {2'd3, 10'd464};
35          13 :sq_root <= {2'd3, 10'd606};
36          14 :sq_root <= {2'd3, 10'd742};
37          15 :sq_root <= {2'd3, 10'd873};
38          default: sq_root <= 12'd0; // reset by default
39      endcase

```

```

40 end
41
42 // continuous assignments for int and decimal parts
43 assign sq_root_int = sq_root [11:10];
44 assign sq_root_dp = sq_root [9:0];
45
46 endmodule

```

To simulate the functionality of this ROM block, I sent in binary values 0000 to 1111 into the circuit to see the values we get out.

```

1  /*
2     chase lotito
3     lab 5 section b
4     rom square root testbench
5  */
6
7  `include "./rom_b.v"
8  `timescale 1us / 1us
9
10 module rom_b_tb();
11
12 // GTKWAVE (waveform simulator)
13 initial begin : GTKWAVE
14     $dumpfile("rom_b.vcd");
15     $dumpvars(0, rom_b_tb);
16 end
17
18 // I/O
19 reg [3:0] n; // signed number
20 wire [11:0] sq_root; // square root of n
21
22 // Initialize the Squarer ROM
23 rom_b U1 (
24     .n(n), .sq_root(sq_root)
25 );
26
27 // Send 4-bit numbers 0000 -> 1111
28 initial begin : stimulus
29
30     // n = 0000 -> 1111
31     for(integer i = 0; i < 16; i = i + 1)
32         #10 n = i;
33
34     #10 $finish;
35 end
36

```

```
37
38 endmodule
```

This gave the following waveforms in GTKWAVE:

 


Figure 2: Square Rooter Circuit Output Waveforms