


# ECE 426/516 Implementation of VLSI Systems with HDL

## Lab 6 Arithmetic Circuit Design with Pipelines

**Due date: May 5<sup>th</sup>, 2024, by 11:30pm**
 
### Section A

In this section, you will code and test a design for adding two signed numbers of width 16 bits each at a time without any pipelining.



### Lab Procedure

1. Use the following module template for this adder design.

// Addition of two 16 bits, 2's complement numbers, n1 and n2. All the 16 bits addition at one stroke without any pipeline. Result is 17 bits.

```
module adder_a (clk, n1, n2, sum) ;  
input clk ;  
input [15:0] n1 ;  
input [15:0] n2 ;  
output [16:0] sum ;
```

```
reg [16:0] sum;  
wire [16:0] sum_i;
```

```
assign sum_i = _____; // Add after sign extension - Result (i).  
always @ (posedge clk) // Pipeline 1, clk (1), register final result (i).  
begin  
    sum <= _____;  
end  
endmodule
```

2. Write a test bench to verify the functionality. Synthesize this design and report the number of gates and operating clock cycle.

## Section B

### Lab Procedure

1. In this section, you add pipeline stage. **8 bits are used at every pipeline stage.** Use the following template to complete your Verilog coding.

// Addition of two 16 bit, 2's complement nos., n1 and n2. 8 bits addition at a time. Result is 17 bits.

```
module adder_b (clk, n1, n2, sum) ;
```

```
input  clk ;
input  [15:0] n1 ;
input  [15:0] n2 ;
output [16:0] sum ;
```

```
reg [16:0]    sum ;
wire [8:0]    sum_LSB ;
reg [8:0]     sum_LSB_1 ;
```

```
reg [15:8]    n1_reg1 ;
reg [15:8]    n2_reg1 ;
```

```
wire  [16:8] sum_MSB ;
wire  [16:0] sum_next ;
```

```
assign sum_LSB = ____ ; // Add least 8 significant bits. sum_LSB [8] is the carry.
```

```
always @ (posedge clk) // Pipeline 1, clk (1), register LSB to continue addition of MSB.
```

```
begin
    sum_LSB_1 <= ____ ;           // Preserve LSB sum
    n1_reg1   <= ____ ;           // Preserve MSBs of n1
    n2_reg1   <= ____ ;           // Preserve MSBs of n2
end
```

```
// Extend sign & add msbs with carry.
```

```
assign sum_MSB = _____; // Add MSBs with carry.
```

```
assign sum_next = _____;
```

```
always @ (posedge clk)      // Pipeline 2, clk (2), register result.
```

```
    begin
```

```
        sum <= _____;
```

```
    end
```

```
endmodule
```

2. Write a test bench to verify the functionality. Synthesize this design and report the number of gates and operating clock cycle.

## **Demo**

You should demo the following aspects of your design to TA.

1. Verilog code of your design
2. Your simulation waveforms and your synthesized results.