


ECE 426/516 Implementation of VLSI Systems with HDL

Lab 5 Design of Memory with Verilog

Due date: April 23, 2024, by 11:30pm

Section A

 In this section, you will design a ROM block, which is designed to realize a simple **squaring circuit**. Implement such a circuit using Verilog for squaring numbers up to 15 if unsigned and -8 to +7 if signed (that means 4-bit input number).



Lab Procedure

1. Use the following module template for this ROM design.

```
// This ROM stores the square of a number n.
module square_ROM (n, sign, square);

input [3:0] n ; // signed number.
input sign ; // signed number if it is high and unsigned otherwise.
output [7:0] square ; // Result = n x n.
reg [7:0] square ;

always @ (n or sign)
begin
if (sign == 0) // Output "square" if the input is unsigned.
begin
case (n)
0 : square <= 0 ;
1 : square <= ____ ;
2 : square <= ____ ;
3 : square <= ____ ;
```

```

4 :   square <= ____ ;
5 :   square <= ____ ;
6 :   square <= ____ ;
7 :   square <= ____ ;
8 :   square <= ____ ;
9 :   square <= ____ ;
10 :  square <= ____ ;
11 :  square <= ____ ;
12 :  square <= ____ ;
13 :  square <= ____ ;
14 :  square <= ____ ;
15 :  square <= 255 ;
      default :    square <= 0 ;      // Clear the result.
endcase
end

else
  begin
case (n)  // Output "square" if the input is signed.
0 :   square <= 0 ;
1 :   square <= 1 ;
2 :   square <= 4 ;
3 :   square <= ____ ;
4 :   square <= ____ ;
5 :   square <= ____ ;
6 :   square <= ____ ;
7 :   square <= ____ ;
8 :   square <= ____ ;
9 :   square <= ____ ;
10 :  square <= ____ ;
11 :  square <= ____ ;
12 :  square <= ____ ;
13 :  square <= ____ ;
14 :  square <= ____ ;
15 :  square <= ____ ;
      default :    square <= 0 ;      // Clear the result.
endcase
end
end
endmodule

```

2. Write a test bench to test your behavioral ROM design by simulating the functionality. Test your unsigned and signed inputs in your test bench.

Section B

In this section, you will design a ROM based **square root circuit** for unsigned numbers in the range of 0 to 15. Provide three digits after decimal point. Such as if the input number is a 2, the output should be the square root of 2, which is 1.414. Complete the following Verilog code and write a test bench and verify your results.

/ This ROM stores the square root of a number n.

```
module square_root_ROM (n, sq_root) ;
```

```
input [3:0] n ; // Unsigned number.
```

```
output [11:0] sq_root ; // Result = Square root of n.
```

```
reg [11:0] sq_root ; // Msb 2 bits (sq_root_int) is the integer part and the  
// other bits (sq_root_dp) are after the decimal point.
```

```
wire [1:0] sq_root_int ;
```

```
wire [9:0] sq_root_dp ;
```

```
always @ (n)
```

```
begin
```

```
case (n) // Output "square root" .
```

```
0 : sq_root <= 0 ;  
1 : sq_root <= _____ ;  
2 : sq_root <= _____ ;  
3 : sq_root <= _____ ;  
4 : sq_root <= _____ ;  
5 : sq_root <= _____ ;  
6 : sq_root <= _____ ;  
7 : sq_root <= _____ ;  
8 : sq_root <= _____ ;  
9 : sq_root <= _____ ;  
10 : sq_root <= _____ ;
```

```

11 : sq_root <= _____ ;
12 : sq_root <= _____ ;
13 : sq_root <= _____ ;
14 : sq_root <= _____ ;
15 : sq_root <= _____ ;

default :    sq_root <= 0 ; // Clear the result.

endcase

end

assign sq_root_int = _____ ;
assign sq_root_dp  = _____ ;

endmodule

```

Demo

You should demo the following aspects of your design to TA.

1. Verilog code for ROM based square and square-root of circuits.
2. Simulation waveforms demonstrating correct functionality of both designs.