

ECE 426/516 Implementation of VLSI Systems with HDL

Homework #1 Review of Combinational and Sequential Logics

Due Date: 11:30pm on January 29th, 2024

Please upload your homework solution to D2L

Question 1: for the combinational circuit shown in Figure 1,

- Write the Boolean expression of T_1 , T_3 , T_4 , F_1 and F_2 in terms of the four input variables A , B , C , D .
- Write the truth table showing binary values of T_1 , T_3 , T_4 , F_1 and F_2 for all combinations of four inputs (A , B , C , D)
- Simplify the functions of F_1 and F_2 by using Karnaugh map method.

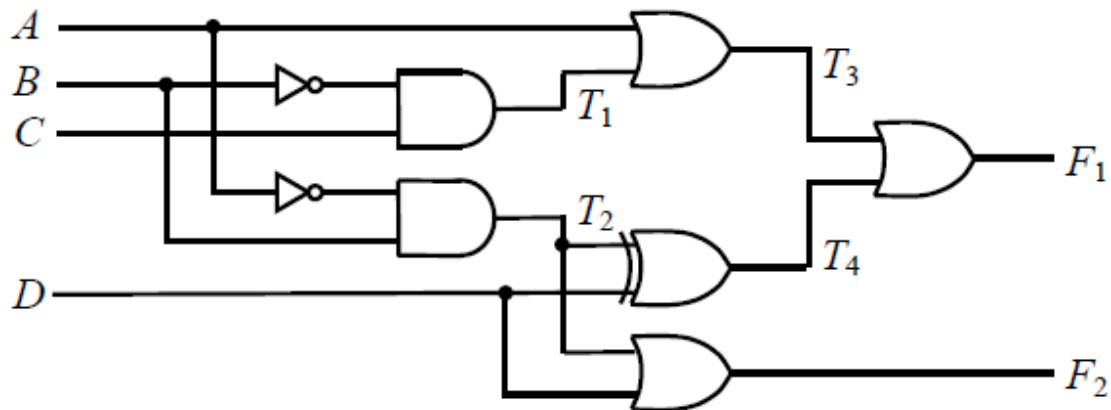


Figure 1. Combinational circuit

Question 2: consider the following sequential building blocks in Figure 2,

- What type of sequential block is it?
- Assume that $S = R = 1$, what happens to the outputs Q and Q' when CLK transitions from a 1 to 0?

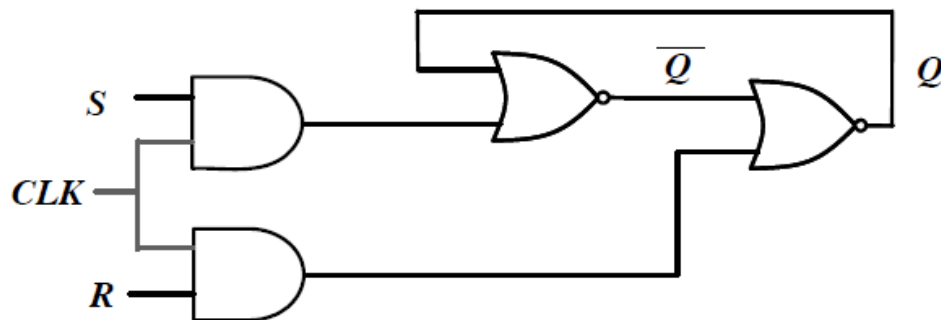


Figure 2 Sequential circuit

Question 3: the circuit in Figure 3 looks like a counter. What is the sequence that this circuit counts in? Complete the timing diagram given in Figure 3. The initial conditions of $Q_0Q_1Q_2$ are 000.

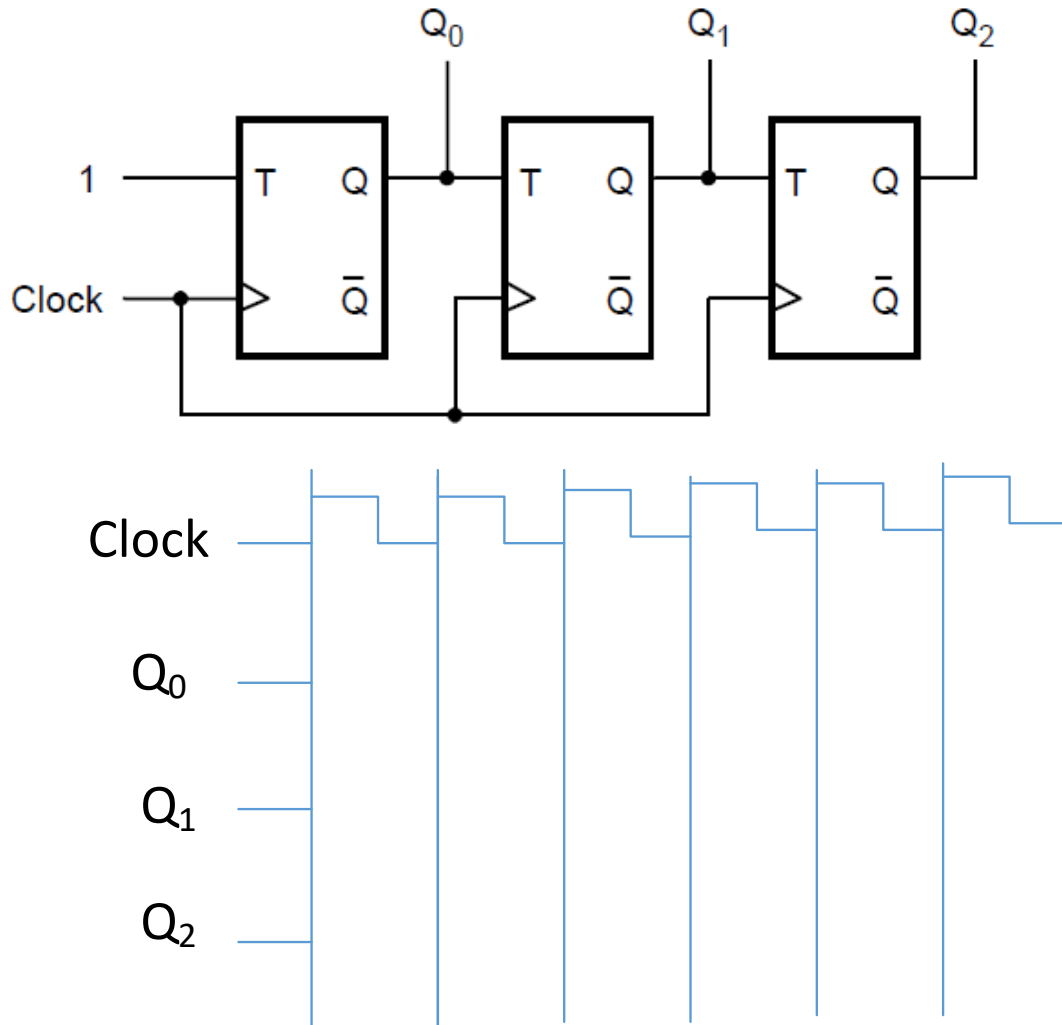


Figure 3. Counter-type circuit

Question 4: you are given the sequential circuit shown in Figure 4. Find the state diagram, state assigned table and state table for the circuit using Mealy-type FSM. Assume the state assignments as $\{A=00, B=01, C=10, D=11\}$.

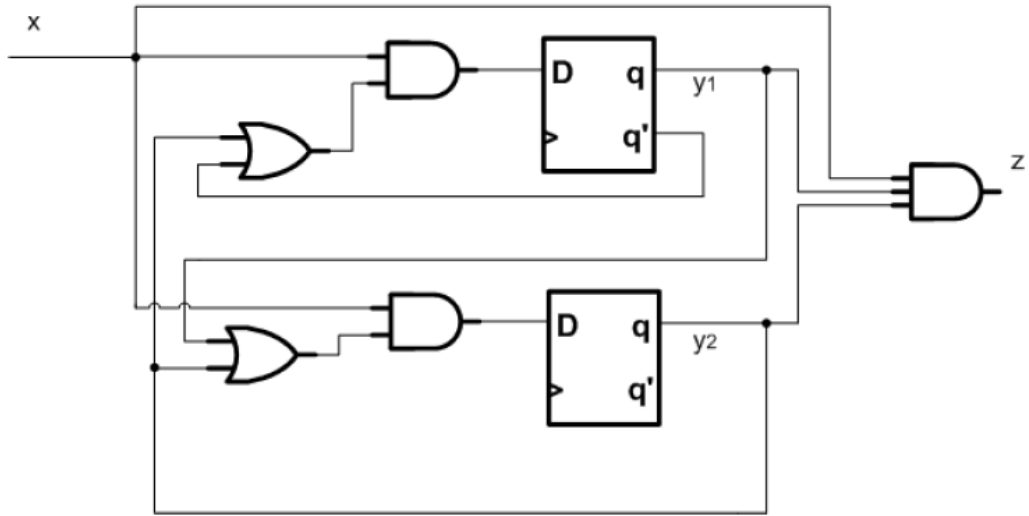


Figure 4. Finite-State Machine circuit