

Arithmetic Circuit Designs with Pipelines

Verilog Lab 6

Chase A. Lotito, *SIUC Undergraduate*

Section A: 16-bit adder without pipelining.

```
1 // chase lotito - ece426 lab 6 - adder a
2
3 // Addition of two 16 bits, 2's complement nos., n1 and n2. All the 16
  bits addition at one stroke without any pipeline.
4 // Result is 17 bits.
5
6 `timescale 1us / 1us
7
8 module adder_a (clk, n1, n2, sum);
9
10 // i/o
11 input clk;
12 input [15:0] n1, n2;
13 output [16:0] sum ;
14
15 reg [16:0] sum;
16 wire [16:0] sum_i;
17
18 assign sum_i = {n1[15], n1} + {n2[15], n2}; // Add after sign
  extension - Result (i).
19
20 // Frequency of operation is not relevant since this is a combination
  circuit.
21 // Pipeline 1, clk (1), register final result (i).
22 always @ (posedge clk) begin
23     sum <= sum_i;
24 end
25
26 endmodule
```

```
1 // Test bench for adder_a design
2
3 `define CLKPERIODBY2 5 // Operate at 50 MHz.
4
5 `timescale 1us / 1us
6 `include "adder_a.v" // This is the design.
7
8 module adder_a_testbench;
9
```

```

10 reg clk;
11 reg [15:0] n1;
12 reg [15:0] n2;
13 wire [16:0] sum;
14
15 adder_a U1 (.clk(clk), .n1(n1), .n2(n2), .sum(sum) );
16
17 // GTKWAVE (waveform simulator)
18 initial begin : GTKWAVE
19     $dumpfile("adder_a.vcd");
20     $dumpvars(0, adder_a_testbench);
21 end
22
23 initial begin // Apply different sets of inputs.
24     clk = 1'b0; n1 = 16'h0; n2 = 16'h0;
25
26     #10 n1 = 16'h0001; n2 = 16'h0101;
27     #10 n1 = 16'h0fff; n2 = 16'h0fff;
28     #10 n1 = 16'h7fff; n2 = 16'h7fff;
29     #10 n1 = 16'h8000; n2 = 16'h8000;
30     #10 n1 = 16'h0001; n2 = 16'h0001;
31     #10 n1 = 16'hffff; n2 = 16'h0001;
32     #10 n1 = 16'h7fff; n2 = 16'h7fff;
33     #10 n1 = 16'h5555; n2 = 16'haaaa;
34     #10 n1 = 16'h0000; n2 = 16'h0000;
35
36     #20 $finish;
37 end
38
39 initial $monitor("[%0t us] clk = %b n1 = %h n2 = %h sum = %h", $time,
    clk, n1, n2, sum);
40
41 always #`CLKPERIODBY2 clk <= ~clk; // Toggle the clock.
42
43 endmodule

```

 


Figure 1: Adder A Waveforms

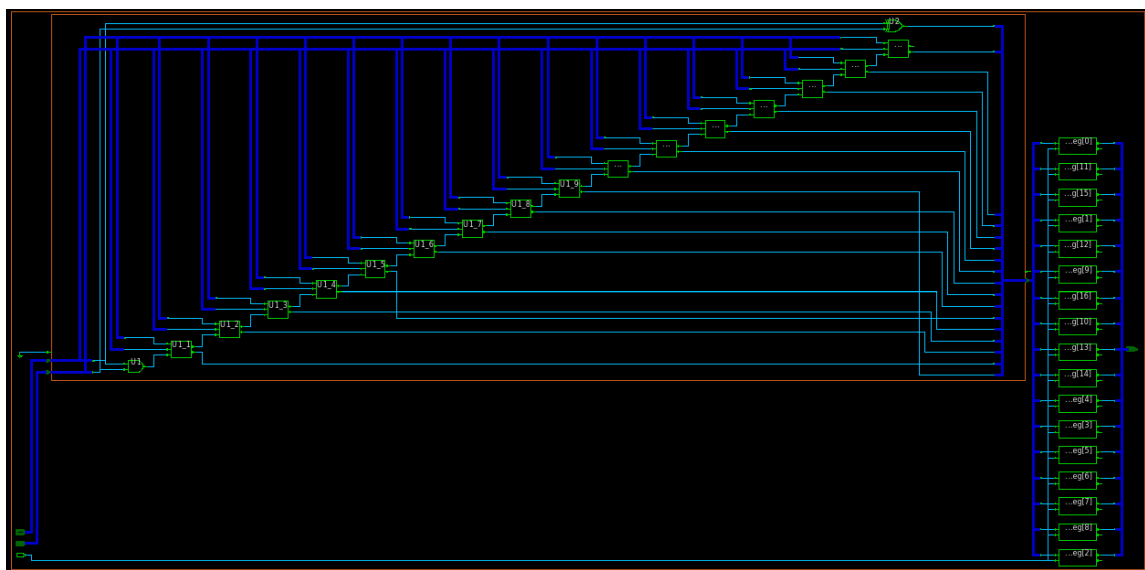


Figure 2: Adder A Circuit

```

*****
Report : area
Design : adder_a
Version: S-2021.06-SP5-4
Date   : Sat Apr 27 16:40:54 2024
*****

Library(s) Used:

    saed90nm_max (File: /synopsys/GPDK/SAED_ED

Number of ports:          103
Number of nets:           135
Number of cells:          37
Number of combinational cells: 18
Number of sequential cells: 17
Number of macros/black boxes: 0
Number of buf/inv:        0
Number of references:      2

Combinational area:      493.055992
Buf/Inv area:            0.000000
Noncombinational area:   423.014395
Macro/Black Box area:    0.000000
Net Interconnect area:   18.859402

Total cell area:         916.070387
Total area:              934.929789
4

```

Figure 3: Adder A Area Report

```

*****
Report : timing
        -path full
        -delay max
        -max_paths 1
Design : adder_a
Version: S-2021.06-SP5-4
Date   : Sat Apr 27 16:41:01 2024
*****

Operating Conditions: WORST   Library: saed90nm_max
Wire Load Model Mode: enclosed

Startpoint: sum_reg[16]
            (rising edge-triggered flip-flop)
Endpoint:  sum[16] (output port)
Path Group: (none)
Path Type: max

Des/Clust/Port      Wire Load Model      Library
-----
adder_a             8000                  saed90nm_max

Point               Incr                Path
-----
sum_reg[16]/CLK (DFFX1)    0.00          0.00 r
sum_reg[16]/Q (DFFX1)     0.63          0.63 f
sum[16] (out)              0.00          0.63 f
data arrival time                    0.63
-----
(Path is unconstrained)

```

Figure 4: Adder A Timing Report

Section B: 16-bit adder with pipelining.

```

1 // chase lotito - ece426 lab 6 - adder b
2 // Addition of two 16 bit, 2's complement nos., n1 and n2. 8 bits
   addition at a time. Result is 17 bits.
3
4 module adder_b ( clk, n1, n2, sum);
5
6 // i/o
7 input clk;
8 input [15:0] n1;
9 input [15:0] n2;
10 output [16:0] sum;
11
12 reg [16:0] sum;
13 wire [8:0] sum_LSB;
14 reg [8:0] sum_LSB_1;
15
16 reg [15:8] n1_reg1;
17 reg [15:8] n2_reg1;
18
19 wire [16:8] sum_MSB;
20 wire [16:0] sum_next;
21
22 assign sum_LSB = n1[7:0] + n2[7:0]; // Add least significant byte.
   sum_LSB [8] is the carry.
23
24 always @ (posedge clk) // Pipeline 1, clk (1), register LSB to
   continue addition of MSB.
25 begin
26     sum_LSB_1 <= sum_LSB;    // Preserve LSB sum
27     n1_reg1 <= n1[15:8];    // Preserve MSBs
28     n2_reg1 <= n2[15:8];
29 end
30
31 // Extend sign & add msbs with carry.
32 assign sum_MSB = {n1_reg1[15], n1_reg1[15:8]} + {n2_reg1[15], n2_reg1
   [15:8]} + sum_LSB_1 [8]; // Add MSBs with carry.
33 assign sum_next = {sum_MSB, sum_LSB_1 [7:0]};
34
35 always @ (posedge clk) // Pipeline 2, clk (2), register result.
36 begin
37     sum <= sum_next;
38 end
39
40 endmodule

```

```

1  // chase lotito - ece426 adder_b testbench
2
3  `define CLKBYPERIOD2 5// Operate at 50 MHz.
4  `include "adder_b.v" // This is the design.
5
6  module adder_b_testbench;
7
8  reg clk;
9  reg [15:0] n1;
10 reg [15:0] n2;
11
12 wire [16:0] sum;
13
14 adder_b U1 (.clk(clk), .n1(n1), .n2(n2), .sum(sum) );
15
16 // GTKWAVE (waveform simulator)
17 initial begin : GTKWAVE
18     $dumpfile("adder_b.vcd");
19     $dumpvars(0, adder_b_testbench);
20 end
21
22 initial begin// Apply different sets of inputs.
23     clk = 1'b0; n1 = 16'h0; n2 = 16'h0;
24
25     #10 n1 = 16'h0001; n2 = 16'h0101;
26     #10 n1 = 16'h0fff; n2 = 16'h0fff;
27     #10 n1 = 16'h7fff; n2 = 16'h7fff;
28     #10 n1 = 16'h8000; n2 = 16'h8000;
29     #10 n1 = 16'h0001; n2 = 16'h0001;
30     #10 n1 = 16'hffff; n2 = 16'h0001;
31     #10 n1 = 16'h7fff; n2 = 16'h7fff;
32     #10 n1 = 16'h5555; n2 = 16'haaaa;
33     #10 n1 = 16'h0000; n2 = 16'h0000;
34
35     #10 $stop;
36     $finish;
37 end
38
39 initial $monitor("[%0t us] clk =%b n1 = %h n2 = %h sum = %h", $time,
40     clk, n1, n2, sum);
41
42 always #`CLKBYPERIOD2 clk <= ~clk;// Toggle the clock.
43
44 endmodule

```

 


Figure 5: Adder B Waveforms

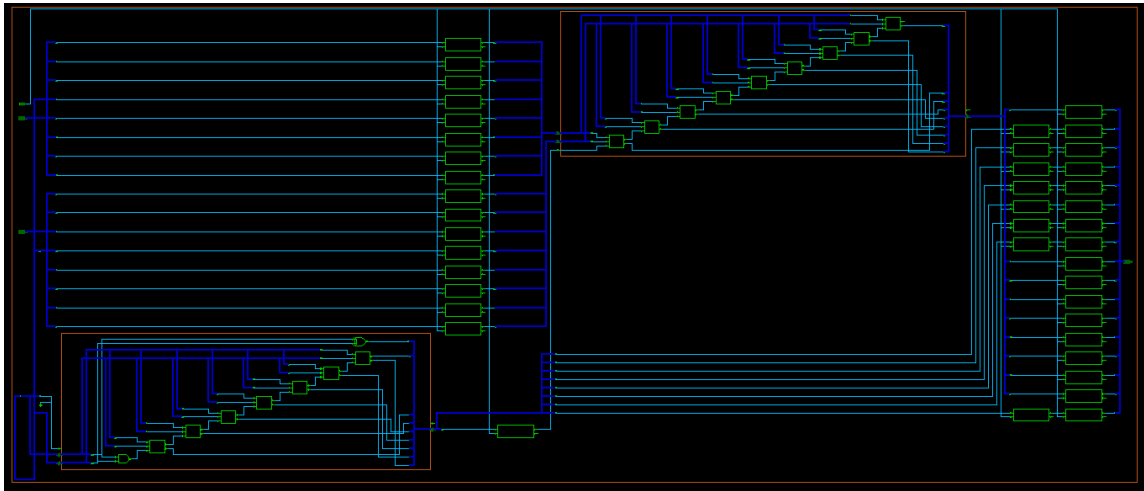


Figure 6: Adder B Circuit


```

*****
Report : area
Design : adder_b
Version: S-2021.06-SP5-4
Date   : Sat Apr 27 16:44:27 2024
*****

Information: Updating design information... (U
Library(s) Used:

    saed90nm_max (File: /synopsys/GPDK/SAED_ED

Number of ports:          108
Number of nets:           162
Number of cells:           63
Number of combinational cells: 18
Number of sequential cells: 42
Number of macros/black boxes: 0
Number of buf/inv:         0
Number of references:      3

Combinational area:        493.055992
Buf/Inv area:              0.000000
Noncombinational area:     1045.094387
Macro/Black Box area:      0.000000
Net Interconnect area:     44.824272

Total cell area:           1538.150379
Total area:                1582.974651
1

```

Figure 7: Adder B Area Report

```

*****
Report : timing
        -path full
        -delay max
        -max_paths 1
Design : adder_b
Version: S-2021.06-SP5-4
Date   : Sat Apr 27 16:44:29 2024
*****

Operating Conditions: WORST   Library: saed90nm_max
Wire Load Model Mode: enclosed

Startpoint: sum_reg[16]
            (rising edge-triggered flip-flop)
Endpoint: sum[16] (output port)
Path Group: (none)
Path Type: max

Des/Clust/Port      Wire Load Model      Library
-----
adder_b             8000                  saed90nm_max

Point              Incr              Path
-----
sum_reg[16]/CLK (DFFX1)      0.00              0.00 r
sum_reg[16]/Q (DFFX1)       0.63              0.63 f
sum[16] (out)                0.00              0.63 f
data arrival time           0.63
-----

```

Figure 8: Adder B Timing Report