

SOUTHERN ILLINOIS UNIVERSITY
CARBONDALE

ECE 426 Implementation of VLSI Systems

Lab 3: Ripple-Carry and Carry-Lookahead Adders

Performed by:

Chase Lotito

856093429

Instructor: Dr. Chao Lu

January 29, 2024

Table of Contents

Ripple-Carry Adder Demo.....	3
Carry-Lookahead Adder Demo.....	7
Appendix A: Ripple-Carry Adder Code	10
Appendix B: Carry-Lookahead Adder Code	14

Ripple-Carry Adder Demo

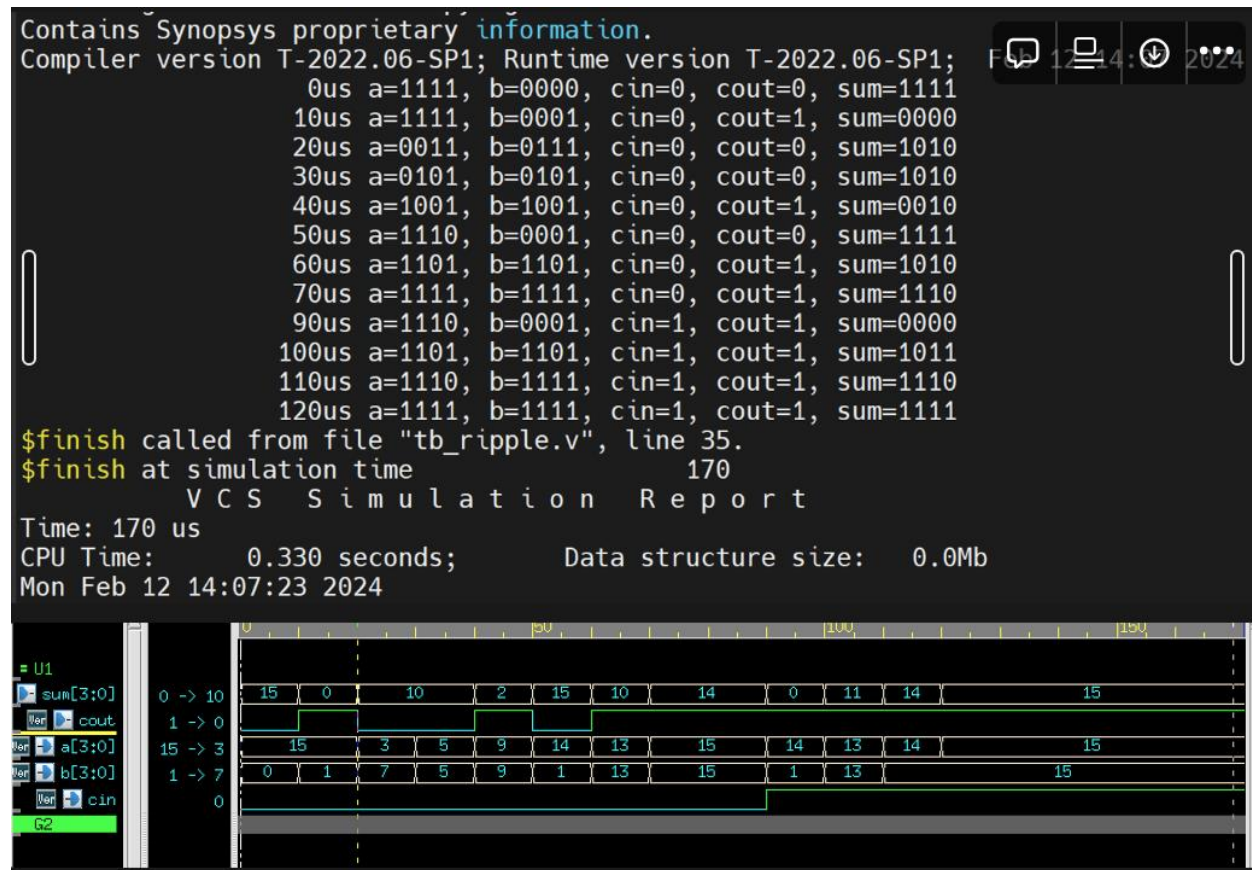


Figure 1: Ripple-Carry Simulation

```

Operating Conditions: WORST   Library: saed90nm_max
Wire Load Model Mode: enclosed

Design      Wire Load Model      Library
-----
RippleCarryAdder_4bit  ForQA      saed90nm_max
FullAdder_0           ForQA      saed90nm_max
FullAdder_1           ForQA      saed90nm_max
FullAdder_2           ForQA      saed90nm_max
FullAdder_3           ForQA      saed90nm_max

Global Operating Voltage = 0.7
Power-specific unit information :
  Voltage Units = 1V
  Capacitance Units = 1.000000ff
  Time Units = 1ns
  Dynamic Power Units = 1uW   (derived from V,C,T units)
  Leakage Power Units = 1pW

  Cell Internal Power = 11.1509 uW   (85%)
  Net Switching Power = 1.9580 uW   (15%)
-----
Total Dynamic Power = 13.1089 uW   (100%)

Cell Leakage Power = 582.1436 nW

Information: report_power power group summary does not include estimated clock tree power. (PWR-789)

Power Group      Internal      Switching      Leakage      Total
Power            Power        Power          Power        Power ( % ) Attrs
-----
io_pad           0.0000       0.0000         0.0000       0.0000 ( 0.00%)
memory           0.0000       0.0000         0.0000       0.0000 ( 0.00%)
black_box        0.0000       0.0000         0.0000       0.0000 ( 0.00%)
clock_network    0.0000       0.0000         0.0000       0.0000 ( 0.00%)
register         0.0000       0.0000         0.0000       0.0000 ( 0.00%)
sequential       0.0000       0.0000         0.0000       0.0000 ( 0.00%)
combinational    11.1509      1.9580         5.8214e+05   13.6910 ( 100.00%)
-----
Total            11.1509 uW   1.9580 uW     5.8214e+05 pW 13.6910 uW
1

```

Figure 2: Ripple-Carry Power

e

```
*****
Report : area
Design : RippleCarryAdder_4bit
Version: S-2021.06-SP5-4
Date   : Mon Feb 12 13:57:37 2024
*****

Information: Updating design information... (UID-85)
Library(s) Used:

    saed90nm_max (File: /synopsys/GPDK/SAED_EDK90nm/Di

Number of ports:          34
Number of nets:          41
Number of cells:         16
Number of combinational cells: 12
Number of sequential cells:  0
Number of macros/black boxes: 0
Number of buf/inv:        0
Number of references:     4

Combinational area:      158.515202
Buf/Inv area:            0.000000
Noncombinational area:   0.000000
Macro/Black Box area:    0.000000
Net Interconnect area:   3.372390

Total cell area:         158.515202
Total area:              161.887591
1
```

Figure 3: Ripple-Carry Area

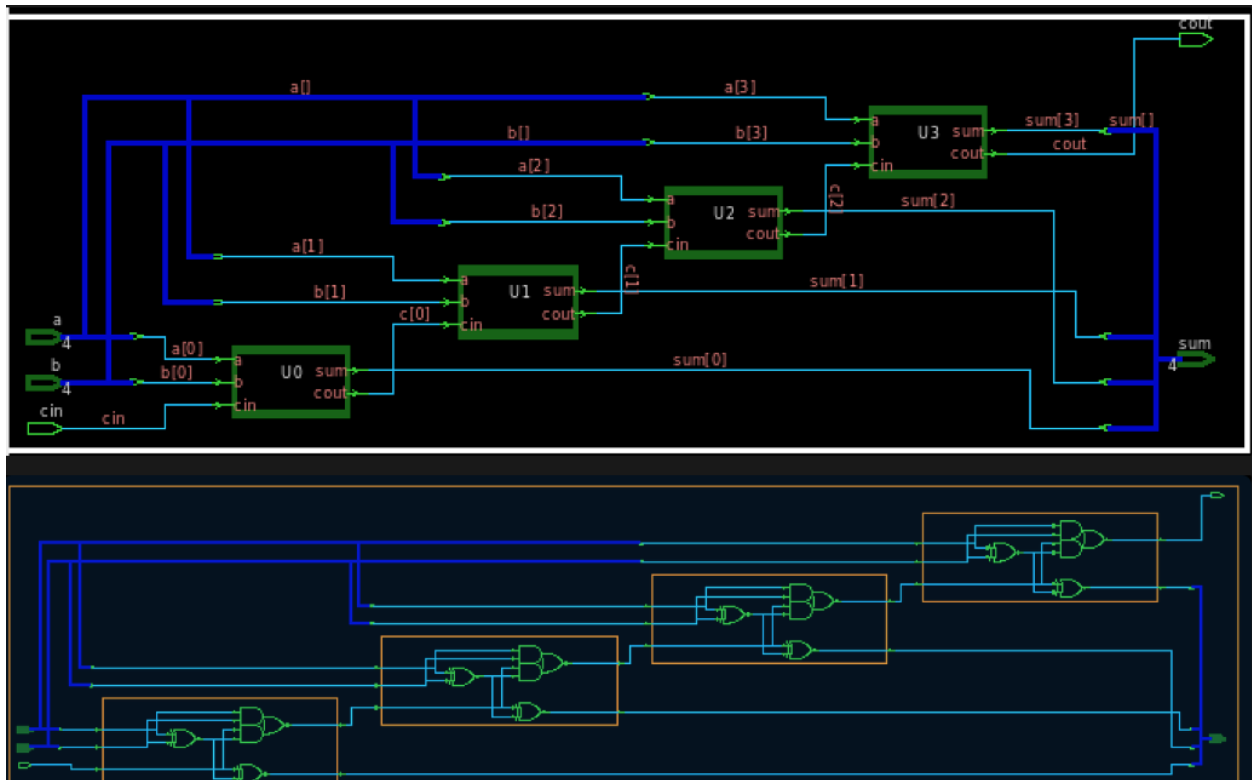


Figure 4: Ripple-Carry Synthesized Circuit

Carry-Lookahead Adder Demo

 


Figure 5: Carry-Lookahead Simulation


```

Operating Conditions: WORST   Library: saed90nm_max
Wire Load Model Mode: enclosed

Design      Wire Load Model      Library
-----
CarryLookAheadAdder_4bit
          ForQA                  saed90nm_max

Global Operating Voltage = 0.7
Power-specific unit information :
  Voltage Units = 1V
  Capacitance Units = 1.000000ff
  Time Units = 1ns
  Dynamic Power Units = 1uW   (derived from V,C,T units)
  Leakage Power Units = 1pW

  Cell Internal Power = 11.0990 uW   (85%)
  Net Switching Power = 1.9429 uW   (15%)
-----
Total Dynamic Power = 13.0420 uW   (100%)
Cell Leakage Power = 582.0499 nW

Information: report_power power group summary does not include estimated clock tree power. (PWR-789)

```

Power Group	Internal Power	Switching Power	Leakage Power	Total Power	(%)	Attrs
io_pad	0.0000	0.0000	0.0000	0.0000	(0.00%)	
memory	0.0000	0.0000	0.0000	0.0000	(0.00%)	
black_box	0.0000	0.0000	0.0000	0.0000	(0.00%)	
clock_network	0.0000	0.0000	0.0000	0.0000	(0.00%)	
register	0.0000	0.0000	0.0000	0.0000	(0.00%)	
sequential	0.0000	0.0000	0.0000	0.0000	(0.00%)	
combinational	11.0990	1.9429	5.8205e+05	13.6240	(100.00%)	
Total	11.0990 uW	1.9429 uW	5.8205e+05 pW	13.6240 uW		

Figure 6: Carry-Lookahead Power

Report : area

Design : CarryLookAheadAdder_4bit

Version: S-2021.06-SP5-4

Date : Mon Feb 12 14:18:42 2024

Library(s) Used:

saed90nm_max (File: /synopsys/GPDK/SAED_EDK90nm)

Number of ports:	14
Number of nets:	21
Number of cells:	12
Number of combinational cells:	12
Number of sequential cells:	0
Number of macros/black boxes:	0
Number of buf/inv:	0
Number of references:	2

Combinational area:	158.515202
Buf/Inv area:	0.000000
Noncombinational area:	0.000000
Macro/Black Box area:	0.000000
Net Interconnect area:	3.372390

Total cell area:	158.515202
Total area:	161.887591

1

Figure 7: Carry-Lookahead Area

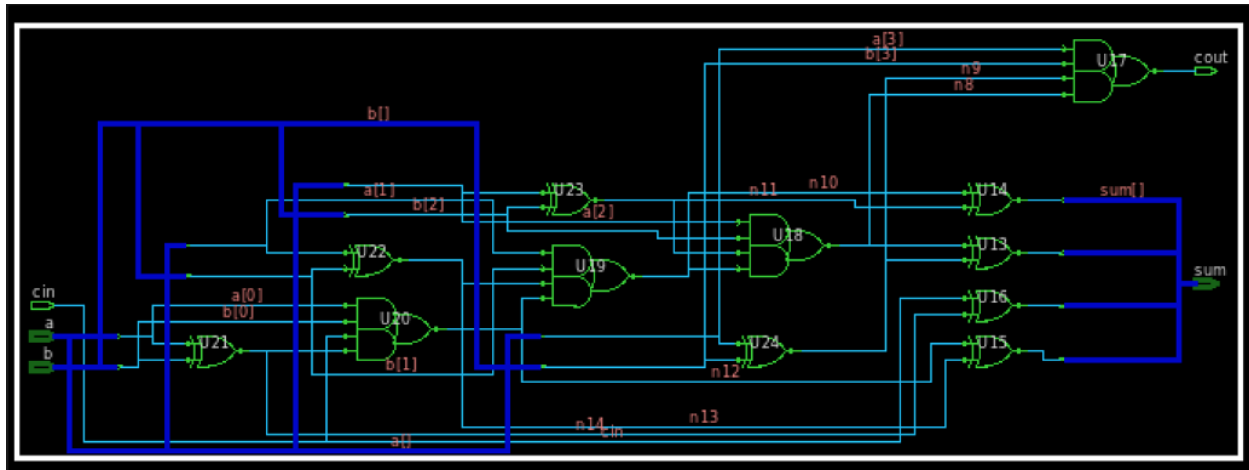


Figure 8: Carry-Lookahead Synthesized Circuit

The only problem is we cannot prove that the Carry-Lookahead is faster just off of power and area reports. We would need to set up a simulation targeted at testing the speed between the two. From QOR reports, we see that the critical path lengths of the circuits are nearly identical, so I'm not sure what to make of that without a specific timing simulation.

The similarities in critical paths are most likely due to the testbenches for each circuit testing over the same time range and the delays of the inputs being the same for both circuits.

Appendix A: Ripple-Carry Adder Code

```
/*
Chase Lotito - SIUC Undergraduate - SP2024
ECE426 - Chao Lu
LAB3 - 4-bit Adders
*/

// 4-BIT RIPPLE-CARRY ADDER

// Full Adder Block

`include "FullAdder.v"
`timescale 1us/1us

module RippleCarryAdder_4bit (
    sum, cout, a, b, cin
);

// I/O
input [3:0] a, b;
input cin;
```

```

output [3:0] sum;
output cout;

// Intermediate wires
wire [3:0] c; // for carries between blocks

FullAdder U0 (
    .sum(sum[0]),
    .cout(c[0]),
    .a(a[0]),
    .b(b[0]),
    .cin(cin)
);
FullAdder U1 (
    .sum(sum[1]),
    .cout(c[1]),
    .a(a[1]),
    .b(b[1]),
    .cin(c[0])
);
FullAdder U2 (
    .sum(sum[2]),
    .cout(c[2]),
    .a(a[2]),
    .b(b[2]),
    .cin(c[1])
);
FullAdder U3 (
    .sum(sum[3]),
    .cout(c[3]),
    .a(a[3]),
    .b(b[3]),
    .cin(c[2])
);

assign cout = c[3];

endmodule

```

```

// Chase Lotito - SIUC Undergrad - Full Adder

`timescale 1us/1us

module FullAdder (

```

```

        sum, cout, a, b, cin
    );

    // I/O
    input a, b, cin;
    output cout, sum;
    reg cout, sum; // used in always procedural block ... must be reg as well

    always @ (a or b or cin) begin
        sum = a ^ b ^ cin;
        cout = (cin & b) | (a & b) | (a & cin);
    end

endmodule

```

```

// Chase Lotito - Lab 3 Testbench

`include "RippleCarryAdder.v"
`timescale 1us / 1us

module tb_ripple ();

    // I/O
    reg [3:0] a, b;
    reg cin;
    wire [3:0] sum;
    wire cout;

    // GTKWAVE
    initial begin : GTKWAVE
        $dumpfile("tb_ripple.vcd");
        $dumpvars(0, tb_ripple);
    end

    initial
    begin
        #0 a = 4'b1111; b = 4'b0000; cin = 1'b0;
        #10 a = 4'b1111; b = 4'b0001; cin = 1'b0;
        #10 a = 4'b0011; b = 4'b0111; cin = 1'b0;
        #10 a = 4'b0101; b = 4'b0101; cin = 1'b0;
        #10 a = 4'b1001; b = 4'b1001; cin = 1'b0;
        #10 a = 4'b1110; b = 4'b0001; cin = 1'b0;
        #10 a = 4'b1101; b = 4'b1101; cin = 1'b0;
        #10 a = 4'b1111; b = 4'b1111; cin = 1'b0;
    end

```

```

    #10 a = 4'b1111; b = 4'b1111; cin = 1'b0;
    #10 a = 4'b1110; b = 4'b0001; cin = 1'b1;
    #10 a = 4'b1101; b = 4'b1101; cin = 1'b1;
    #10 a = 4'b1110; b = 4'b1111; cin = 1'b1;
    #10 a = 4'b1111; b = 4'b1111; cin = 1'b1;
    #50 $finish;
end

//instantiate the module into the test bench
RippleCarryAdder_4bit U1 (
    .a(a),
    .b(b),
    .cin(cin),
    .sum(sum),
    .cout(cout)
);

initial
begin
    $monitor ($time, "us a=%b, b=%b, cin=%b, cout=%b, sum=%b", a, b, cin, cout,
sum);
end

endmodule

```

```

set search_path ".
/synopsys/GPDK/SAED_EDK90nm/Digital_Standard_Cell_Library/synopsys/models"
set link_library "saed90nm_max.db"
set target_library "saed90nm_max.db"
set symbol_library "saed90nm_max.db"
analyze -library WORK -format verilog
{/home/ugrad/siu856093429/ECE426/lab3/RippleCarryAdder.v}
elaborate RippleCarryAdder_4bit -library WORK
link
compile -exact_map

```

Appendix B: Carry-Lookahead Adder Code

```
// Chase Lotito - SIUC Undergrad - SP2024
// Lab 3 - Part 2 - Carry-Lookahead Adder

// CARRY LOOK AHEAD ADDER USES:
//  $c[i] = g[i] \mid p[i] \& c[i-1]$  ( $c[-1] = \text{cin}$ )
// G is CARRY GENERATE -->  $g = a[i] \& b[i]$ 
// P is CARRY PROPAGATE -->  $p[i] = a[i] \wedge b[i]$  (xor)
// THE SUM:
//  $\text{sum}[i] = p[i] \wedge c[i-1] = a[i] \wedge b[i] \wedge c[i-1]$ 
//

`timescale 1us/1us

module CarryLookAheadAdder_4bit (
    sum, cout, a, b, cin
);

// I/O
input [3:0] a, b;
input cin;
output [3:0] sum;
output cout;

// Interconnections!
wire [3:0] c, g, p; // carries, generates, propogates

// Generate carry bits
assign g[0] = a[0] & b[0];
assign g[1] = a[1] & b[1];
assign g[2] = a[2] & b[2];
assign g[3] = a[3] & b[3];

// Propagate carry bits
assign p[0] = a[0] ^ b[0];
assign p[1] = a[1] ^ b[1];
assign p[2] = a[2] ^ b[2];
assign p[3] = a[3] ^ b[3];

// Carry bits
assign c[0] = g[0] | ( p[0] & cin );
assign c[1] = g[1] | ( p[1] & c[0] );
assign c[2] = g[2] | ( p[2] & c[1] );
```

```
assign c[3] = g[3] | ( p[3] & c[2] );
assign cout = c[3];
```

```
// Sum bits
assign sum[0] = p[0] ^ cin;
assign sum[1] = p[1] ^ c[0];
assign sum[2] = p[2] ^ c[1];
assign sum[3] = p[3] ^ c[2];

endmodule
```

```
// Chase Lotito - Lab 3 Testbench - Carry Lookahead
```

```
`include "CarryLookAheadAdder.v"
`timescale 1us / 1us

module tb_lookahead ();

// I/O
reg [3:0] a, b;
reg cin;
wire [3:0] sum;
wire cout;

// GTKWAVE
initial begin : GTKWAVE
    $dumpfile("tb_lookahead.vcd");
    $dumpvars(0, tb_lookahead);
end

initial
begin
    #0 a = 4'b1111; b = 4'b0000; cin = 1'b0;
    #10 a = 4'b1111; b = 4'b0001; cin = 1'b0;
    #10 a = 4'b0011; b = 4'b0111; cin = 1'b0;
    #10 a = 4'b0101; b = 4'b0101; cin = 1'b0;
    #10 a = 4'b1001; b = 4'b1001; cin = 1'b0;
    #10 a = 4'b1110; b = 4'b0001; cin = 1'b0;
    #10 a = 4'b1101; b = 4'b1101; cin = 1'b0;
    #10 a = 4'b1111; b = 4'b1111; cin = 1'b0;
    #10 a = 4'b1111; b = 4'b1111; cin = 1'b0;
    #10 a = 4'b1110; b = 4'b0001; cin = 1'b1;
    #10 a = 4'b1101; b = 4'b1101; cin = 1'b1;
    #10 a = 4'b1110; b = 4'b1111; cin = 1'b1;
end
```



```

    #10 a = 4'b1111; b = 4'b1111; cin = 1'b1;
    #50 $finish;
end

//instantiate the module into the test bench
CarryLookAheadAdder_4bit U1 (
    .a(a),
    .b(b),
    .cin(cin),
    .sum(sum),
    .cout(cout)
);

initial
begin
    $monitor ($time, "us a=%b, b=%b, cin=%b, cout=%b, sum=%b", a, b, cin, cout,
sum);
end

endmodule

```

```

set search_path ".
/synopsys/GPDK/SAED_EDK90nm/Digital_Standard_Cell_Library/synopsys/models"
set link_library "saed90nm_max.db"
set target_library "saed90nm_max.db"
set symbol_library "saed90nm_max.db"
analyze -library WORK -format verilog
{/home/ugrad/siu856093429/ECE426/lab3/CarryLookAheadAdder.v}
elaborate CarryLookAheadAdder_4bit -library WORK
link
compile -exact_map

```