

1.) A three-phase system has a line-to-line voltage

$$V_{BA} = 1414 \angle -15^\circ \text{ V rms}$$

with a Y load. Find the phase voltages when the phase sequence is *abc*.

2.) A Y-connected source and load are shown in Figure 1. (a) Determine the rms value of the current $i_A(t)$. (b) Determine the average and reactive power delivered to the load.

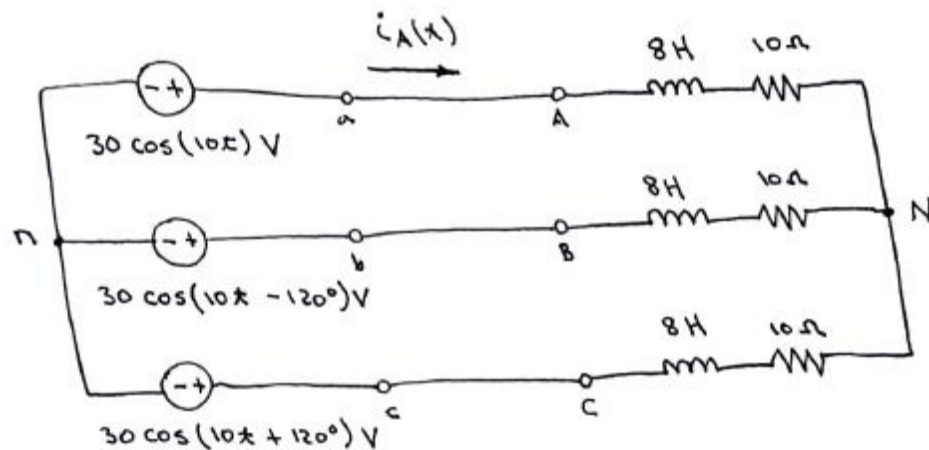


Figure 1

3.) An unbalanced Y-Y circuit is shown in Figure 2. Find the complex power delivered to the load.

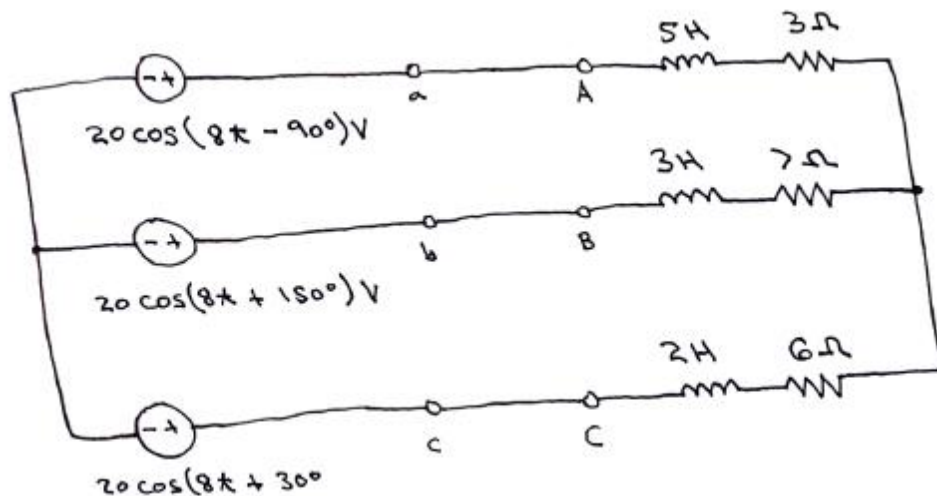


Figure 2

- 4.) An unbalanced four-wire Y-Y circuit is shown in Figure 3. (a) Find the line currents i_a , i_b , i_c , and i_n . (b) Find the complex power absorbed by each phase of the load.

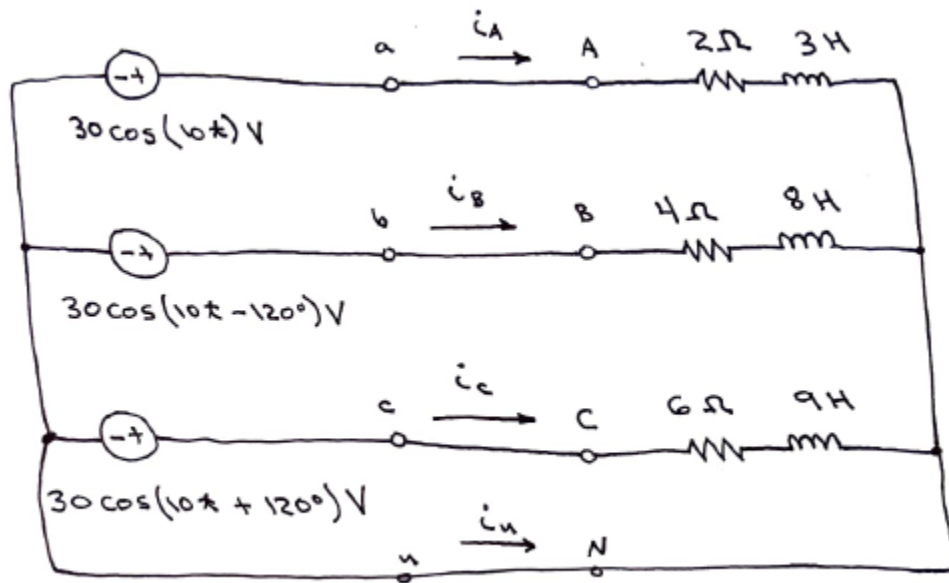


Figure 3

- 5.) A three-phase circuit has two parallel balanced Δ loads, one of $33\text{-}\Omega$ resistors and one of $47\text{-}\Omega$ resistors. Find the magnitude of the total line current when the line-to-line voltage is 220 V rms .

- 6.) A balanced Δ -connected load is connected by three wires, each with a $12\text{-}\Omega$ resistance, to a Y source with

$$\mathbf{V}_a = (480/\sqrt{3})\angle -30^\circ \text{ V rms}, \mathbf{V}_b = (480/\sqrt{3})\angle -150^\circ \text{ V rms}, \text{ and } \mathbf{V}_c = (480/\sqrt{3})\angle 90^\circ \text{ V rms}.$$

Find the line current \mathbf{I}_A when $\mathbf{Z}_\Delta = 16\angle -75^\circ \Omega$.

7.) For the three-phase circuit shown in Figure 4 determine $i(t)$ and the total complex power delivered by the three-phase source.

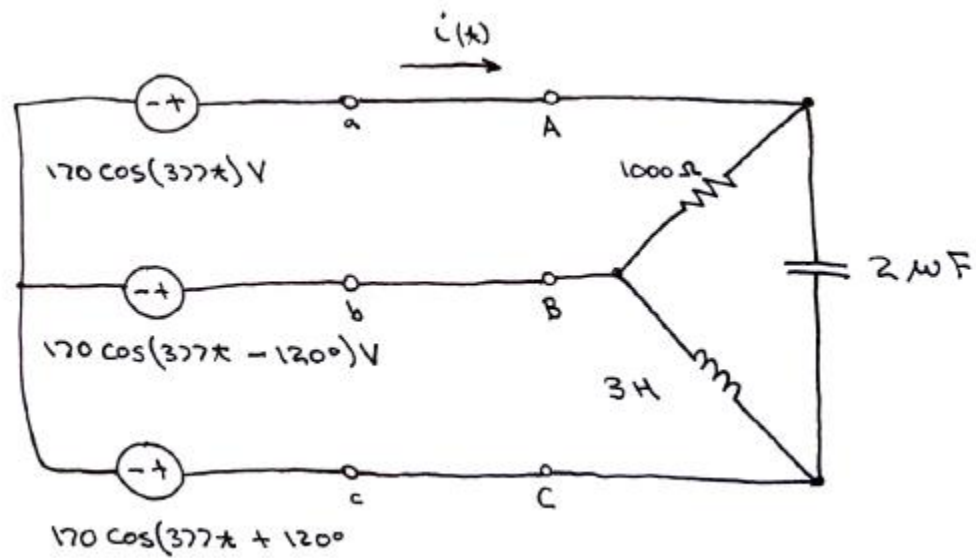


Figure 4